

USB Audio 2.0 - USB VBUS Design Advisory

Document Revision DAUSBAUDIO2110711R

Publication Date: 2011/07/13

Copyright © 2011 XMOS Limited, All Rights Reserved.

XMOS® CONFIDENTIAL

Introduction

The XR-USB-AUDIO-2.0 and XR-USB-AUDIO-2.0-MC reference designs use an SMSC USB3318 USB Transceiver.

This part has a VBUS monitor pin which is connected to the VBUS pin of the USB connector via a resistor. This resistor is used to protect the SMSC part against over-voltage transients.

XMOS has identified a problem when the voltage at the VBUS pin of the USB3318 is near the internal threshold for VbusValid (4.4V min, 4.58V typical, 4.75V max). When this condition occurs, packets are sent continuously on the ULPI bus which affects system operation (causing possible audio glitches etc.)

Solution

The XMOS reference designs use a resistor value of 1k Ω for this VBUS resistor. By increasing the value of this resistor to 20k Ω , the internal pulldown on the VBUS pin within the USB3318 (40-100k Ω) ensures the voltage on the VBUS pin can never be near the internal VbusValid threshold for all valid USB VBUS voltages.

This note therefore advises that this resistor on VBUS is changed from 1k Ω to 20k Ω in all USB device applications.



Copyright © 2011 XMOS Limited, All Rights Reserved.

XMOS Limited is the owner or licensee of this design, code, or Information (collectively, the "Information") and is providing it to you "AS IS" with no warranty of any kind, express or implied and shall have no liability in relation to its use. XMOS Limited makes no representation that the Information, or any particular implementation thereof, is or will be free from any claims of infringement and again, shall have no liability in relation to any such claims.

XMOS and the XMOS logo are registered trademarks of XMOS Limited in the United Kingdom and other countries, and may not be used without written permission. All other trademarks are property of their respective owners. Where those designations appear in this book, and XMOS was aware of a trademark claim, the designations have been printed with initial capital letters or in all capitals.
